
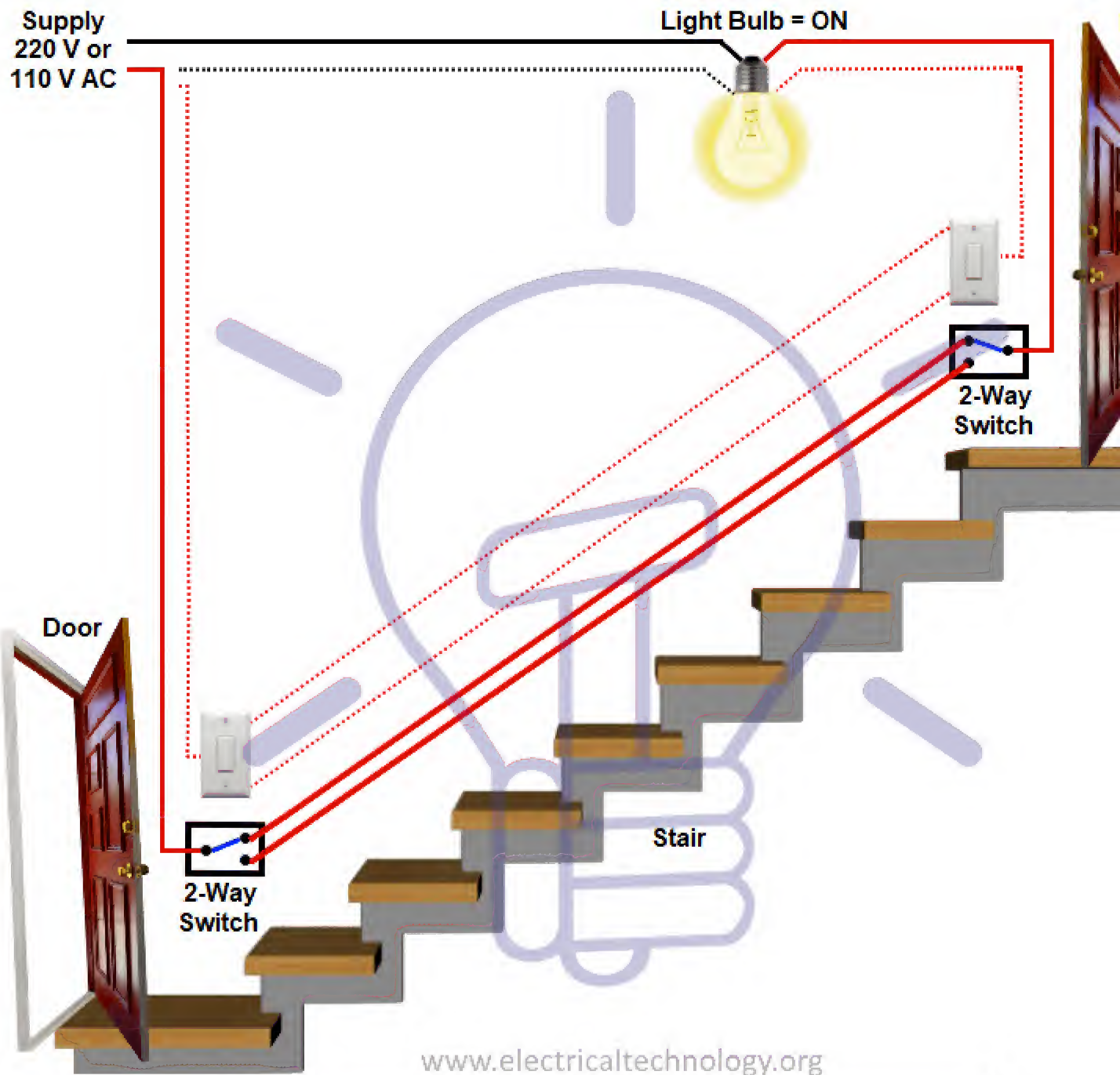



Earth's Omitted For Clarity

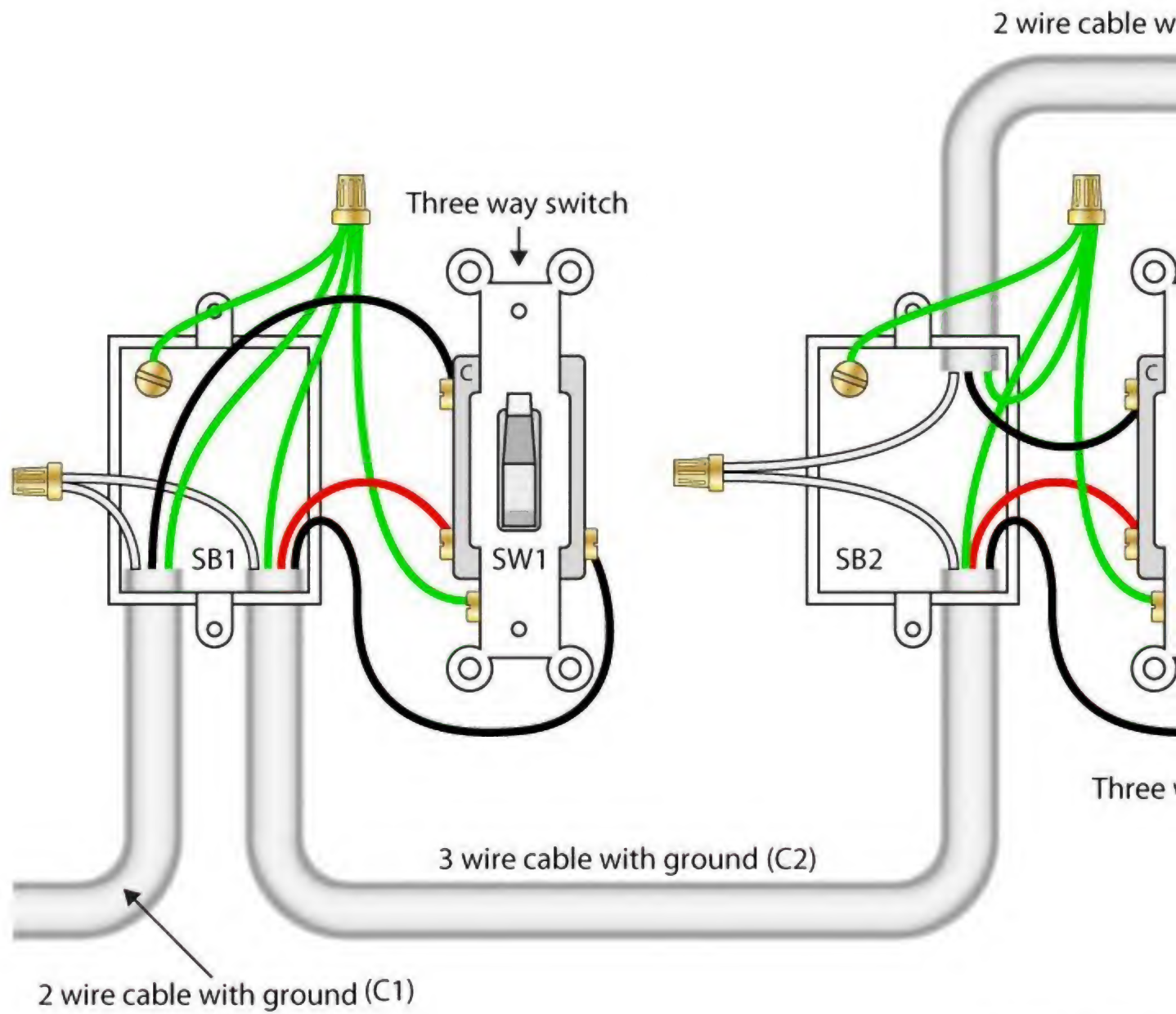

Staircase Wiring Circuit Diagram

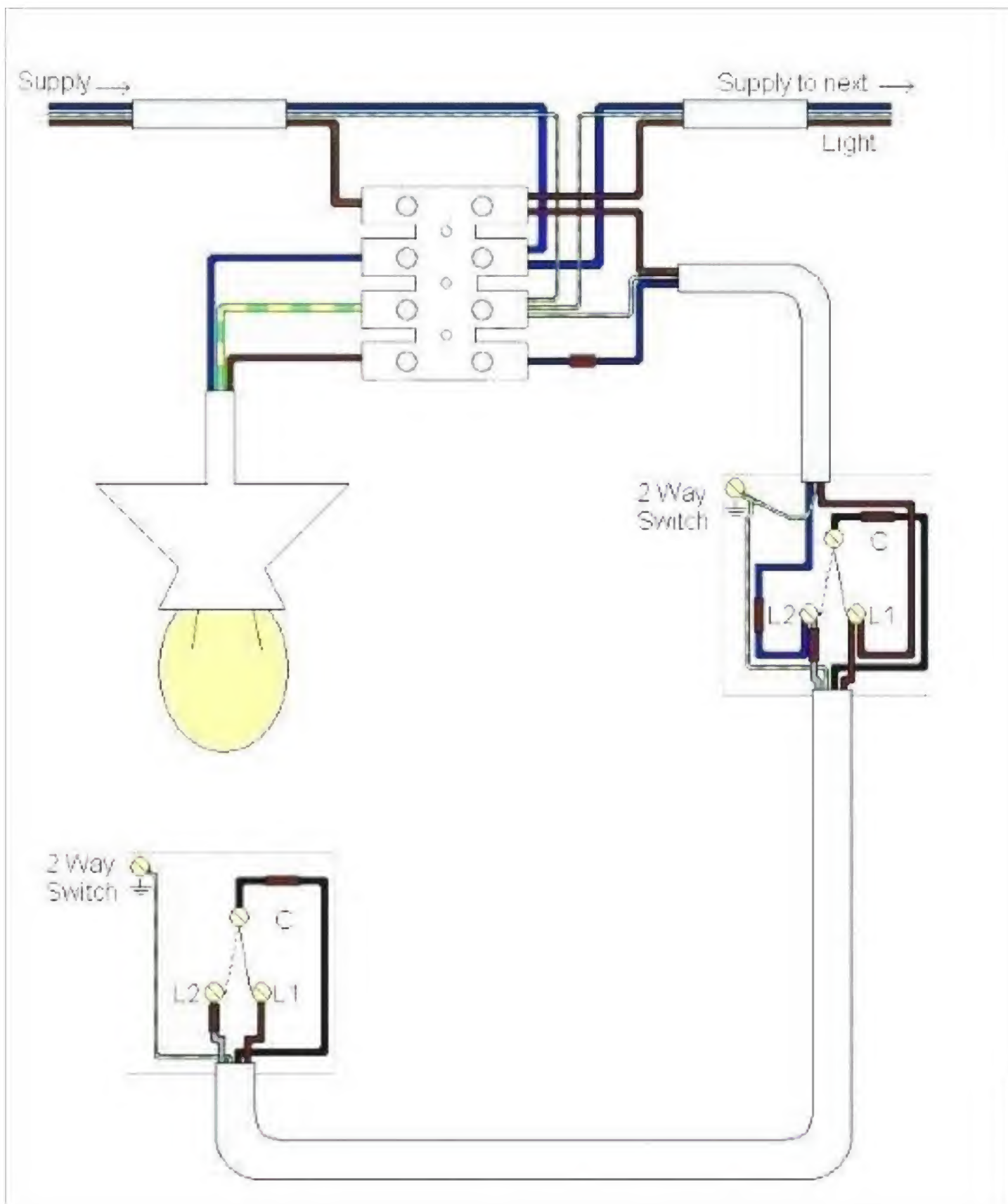How to Control a Lamp from Two Different Places by Two 2-Way Switches





Protective earth
conductors
omitted for clarity

Multiple lamps
switched

Lights switch from multiple
locations using a pair of two
way switches, and any
number of additional
intermediate switches

